

High Frequency Performance of Common-Emitter Amplifier

Design:

1 - Design of CE amplifier, $I_{CQ} = 10 \text{ mA}$ and the output ac resistance, R_o , is 470Ω .

$I_{R1} = 10 I_{BQ}$, and $I_{R2} = 9 I_{BQ}$ for a robust DC stability take $V_E = 2.7 \text{ V}$ and $\beta = 100$.

$$I_B = \frac{I_C}{\beta} = \frac{10 \text{ mA}}{100} = 0.1 \text{ mA}$$

$$I_{R1} = 10 I_B = 1 \text{ mA}$$

$$I_{R2} = 9 I_B = 0.9 \text{ mA}$$

$$R_1 = \frac{V_{CC} - V_B}{I_{R1}} \Rightarrow \frac{12 \text{ V} - 3.7 \text{ V}}{1 \text{ mA}} = 8.6 \text{ k}\Omega$$

$$R_2 = \frac{V_B}{I_{R2}} \Rightarrow \frac{3.7 \text{ V}}{0.9 \text{ mA}} = 3.8 \text{ k}\Omega$$

$$R_E = \frac{V_E}{I_C} \Rightarrow \frac{2.7 \text{ V}}{10 \text{ mA}} = 270 \Omega$$

$$R_o = R_C = 470 \Omega$$

2 - mid-band frequency small signal voltage gain, A_v , and the input impedance R_{in} of the amplifier.

$$g_m = \frac{I_C}{V_T} = 0.4 \text{ S}$$

$$r_\pi = \frac{\beta}{g_m} = 250 \Omega$$

$$R_{in} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{r_\pi} \right)^{-1} = 230 \Omega$$

$$A_v = \frac{V_o}{V_i} = -g_m R_o = -188$$

3 - input capacitance C_{in} of the amplifier using the miller effect method.

Datasheet Values:

$$C_{\mu} = C_{CB} = 8\text{PF (Collector to Base small signal capacitance)}$$

$$f_T = 300\text{ MHz (Transient Frequency where } A_v = 1)$$

$$V_T = 25\text{ mV (Thermal Voltage)}$$

Calculations:

$$C_{\pi} = \frac{g_m}{2\pi f_T} - C_{\mu} = 204\text{ pf}$$

$$C_{in} = C_{\pi} + (1 + A_v)C_{\mu} = 1724\text{ pf}$$

$$C_{out} = \frac{A_v + 1}{A_v} C_{\mu} = 8\text{ pf}$$



$$T_{out} = (R_C || R_L)C_{out} = R_C C_{out} = 3.76\text{ ns}$$

$$T_{in} = \left(\frac{1}{R_g} + \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{r_{\pi}} \right)^{-1} C_{in} = 265\text{ ns}$$

$$H(j\omega) = \frac{A_v z_{in}}{z_{in} + R_g} \left(\frac{1}{(1 + j\omega T_{in})(1 + j\omega T_{out})} \right)$$

$$f_{cutoff} = \frac{1}{2\pi T_{in}} = 650.5\text{ kHz}$$

Simulation Results:

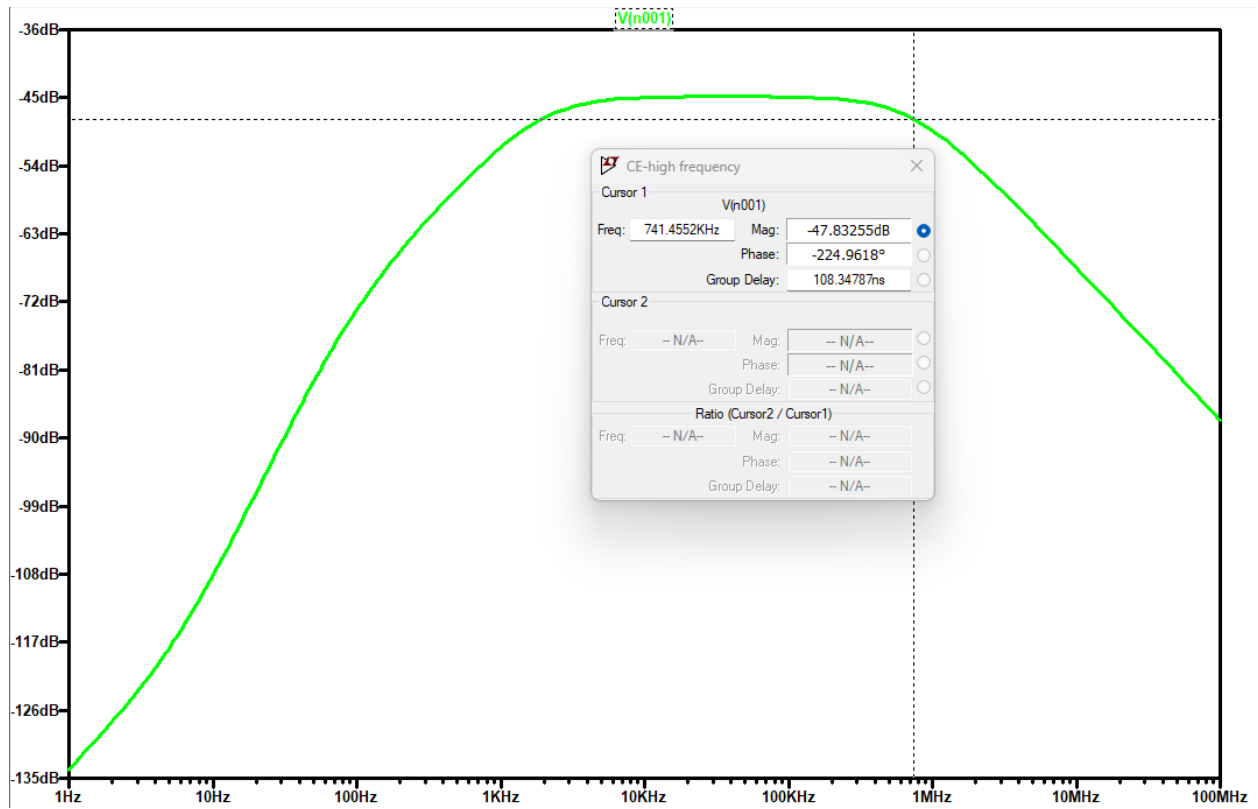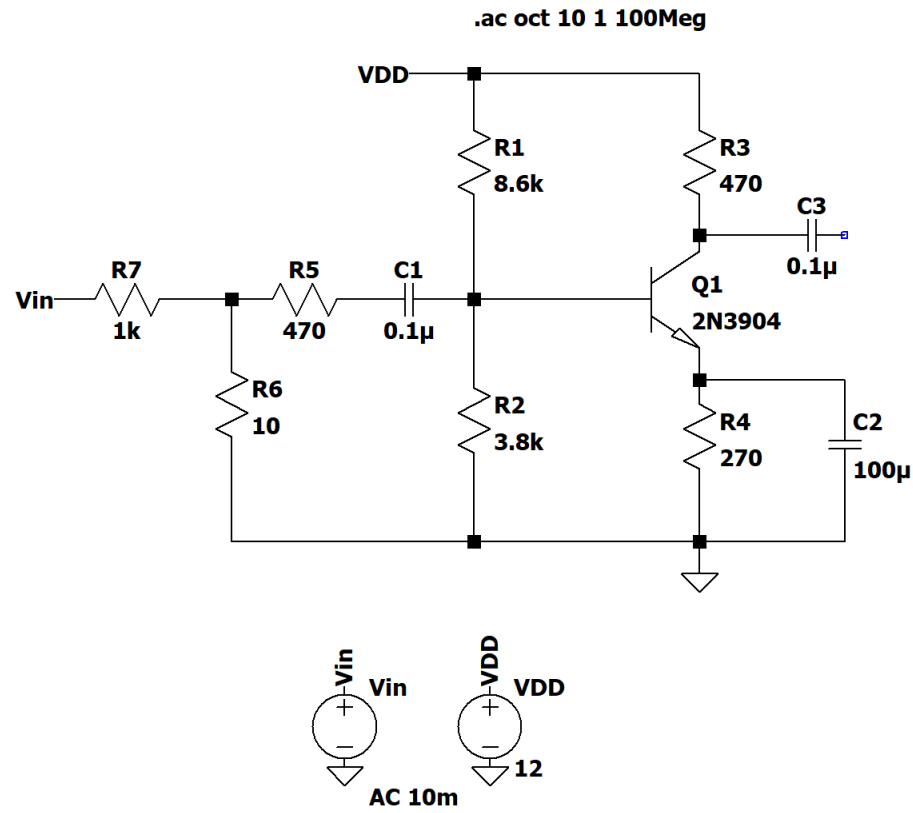

Measured High-Frequency Response of CE Amplifier

Frequency (kHz)	10	50	100	200	400	540	700	1000	2000	3000	4000	6000	8000
v_o (mVpp)	860	860	860	820	700	610	520	400	220	160	125	95	75
v_g (mVpp)	15	15	15	15	15	15	15	15	15	15	15	15	15
$A_g = v_o/v_g$	57.3	57.3	57.3	54.7	46.7	40.7	34.7						

Results:

Method	Description	Upper Cutoff Frequency f_H
Hand Analysis	Dominant-pole estimate using Miller-effect input capacitance	≈ 600 kHz
LTspice Simulation	AC sweep with cursor-based -3 dB extraction	≈ 740 kHz
Experimental Measurement	Gain–frequency sweep using signal generator and oscilloscope	≈ 540 kHz

Results Summary:

The common-emitter amplifier exhibited Miller-effect-limited bandwidth, with an analytically estimated upper cutoff frequency of approximately 600 kHz, a simulated cutoff of approximately 740 kHz, and a measured cutoff of approximately 540 kHz. The close agreement confirms that Miller multiplication of the base–collector capacitance dominates the high-frequency response, motivating cascode topologies for bandwidth improvement.